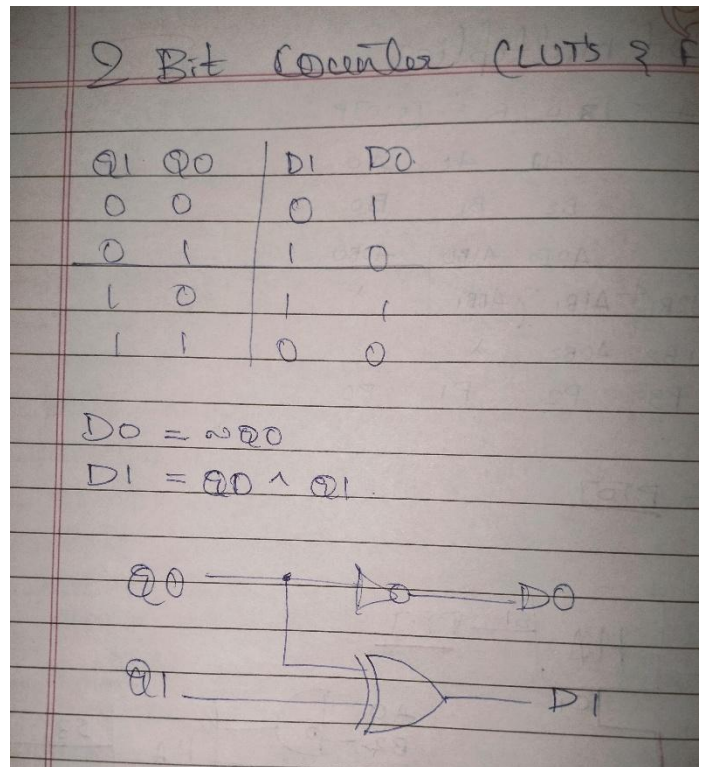


2-Bit Counter


```
//Verilog code for 2-Bit Counter
module counter_2bit (clk, reset, count);
    input wire clk;
    input wire reset;
    output reg [1:0] count;
    wire d0, d1;

    assign d0 = ~count[0];
    assign d1 = count[1] ^ count[0];

    always @(posedge clk) begin
        if (reset)
            count <= 2'b00;
        else
            count <= {d1, d0};
        end
    end
endmodule
```



Waveform:

 

Synthesis analysis schematic:

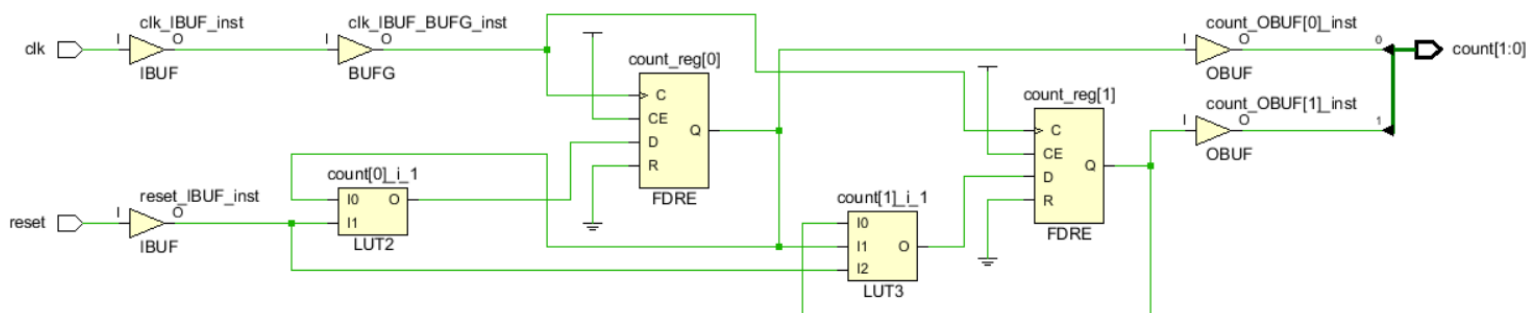


Figure 1: Synthesis analysis schematic

RTL analysis schematic:

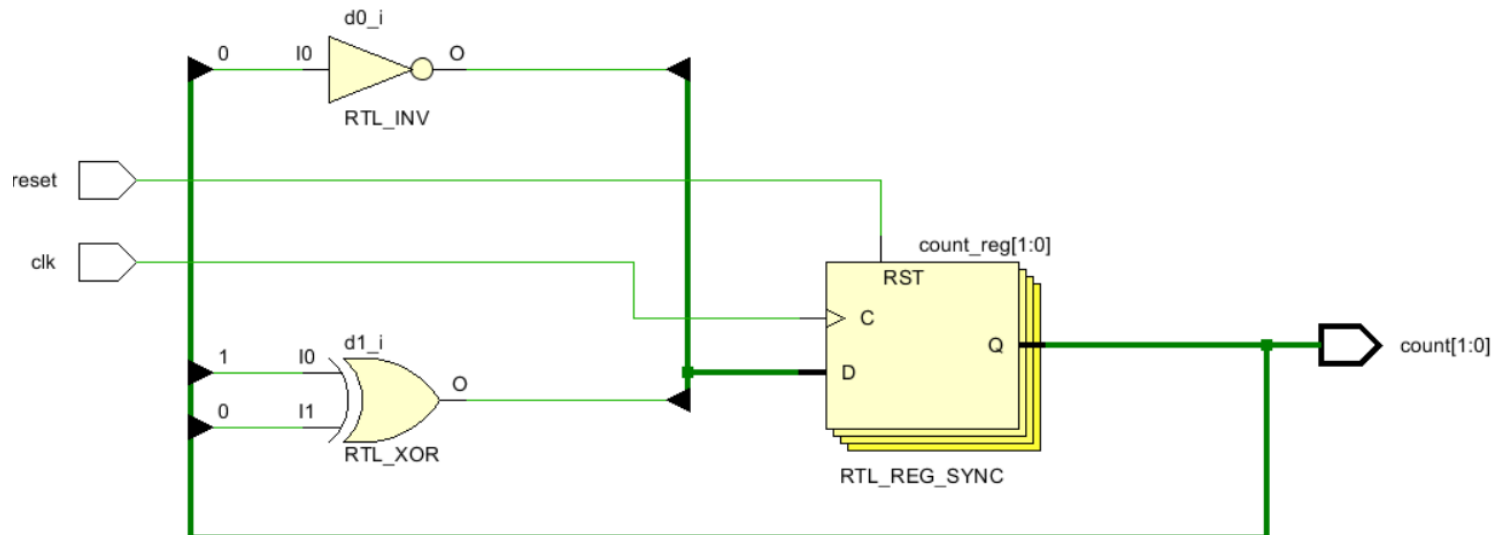


Figure 2: RTL analysis schematic

Look Up Tables:

Cell Properties		
count[0]_i_1		
I1	I0	O=!!I0 & !!I1
0	0	1
0	1	0
1	0	0
1	1	0

Table 1: LUT2

Cell Properties			
count[1]_i_1			
I2	I1	I0	O=I0 & !I1 & !I2 + !I0 & I1 & !I2
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Table 2: LUT3