

2-Bit Counter as a Clock Divider

//Verilog code

```
module counter_clk_div (clk, reset, clk_div2, clk_div4);
```

```
    input wire clk;
```

```
    input wire reset;
```

```
    output wire clk_div2;
```

```
    output wire clk_div4;
```

```
    reg [1:0] count;
```

```
    always @(posedge clk or posedge reset) begin
```

```
        if (reset)
```

```
            count <= 2'b00;
```

```
        else
```


```
            count <= count + 1;
```

```
    end
```


```
    assign clk_div2 = count[0];
```

```
    assign clk_div4 = count[1];
```


```
endmodule
```

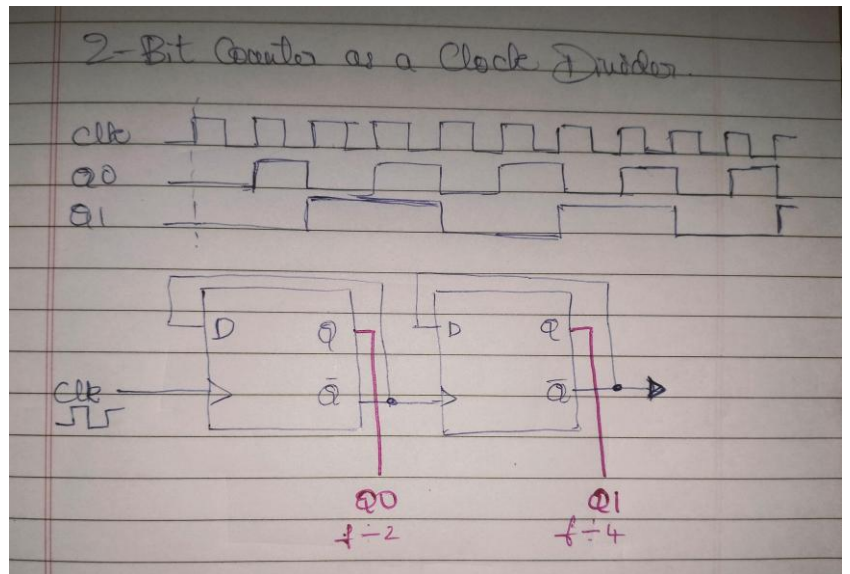


Waveform:

 

Synthesis schematic:

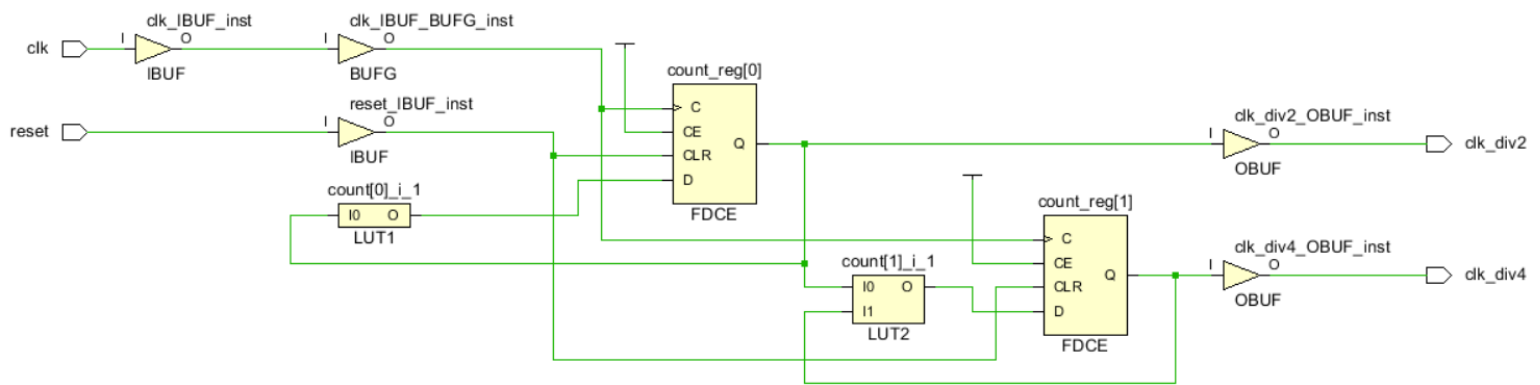

RTL Analysis schematic:

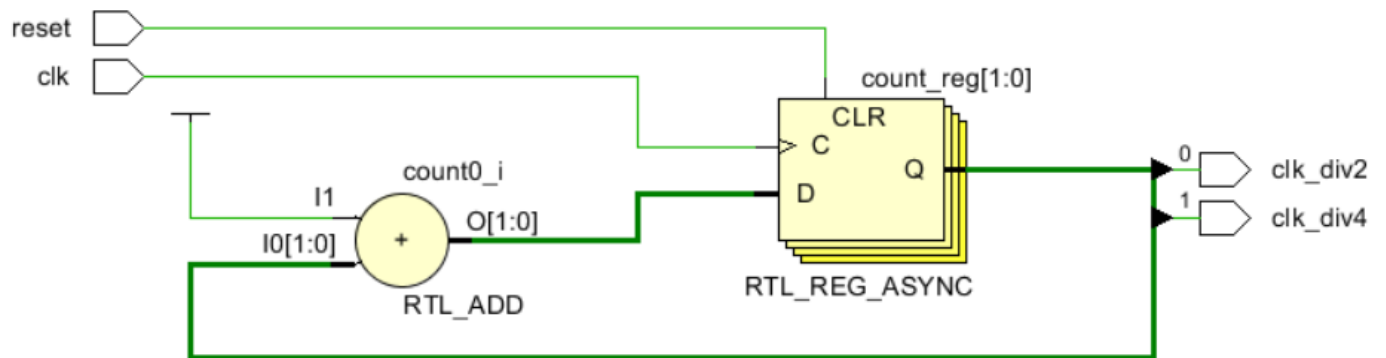

Look Up Tables:

Cell Properties		
count[0]_i_1		
I0	O=!I0	
0	1	
1	0	

Table 1: LUT1

Cell Properties		
count[1]_i_1		
I1	I0	O=I0 & !I1 + !I0 & I1
0	0	0
0	1	1
1	0	1
1	1	0

Table 2: LUT2